

CECS 311 - LAB 5

BJT Common Emitter Amplifier


NAME:

POSSIBLE POINTS: 10

COURSE DATE & TIME:

The Following is an example of a BJT used in a Common Emitter Amplifier circuit.

Part 1 – Calculation

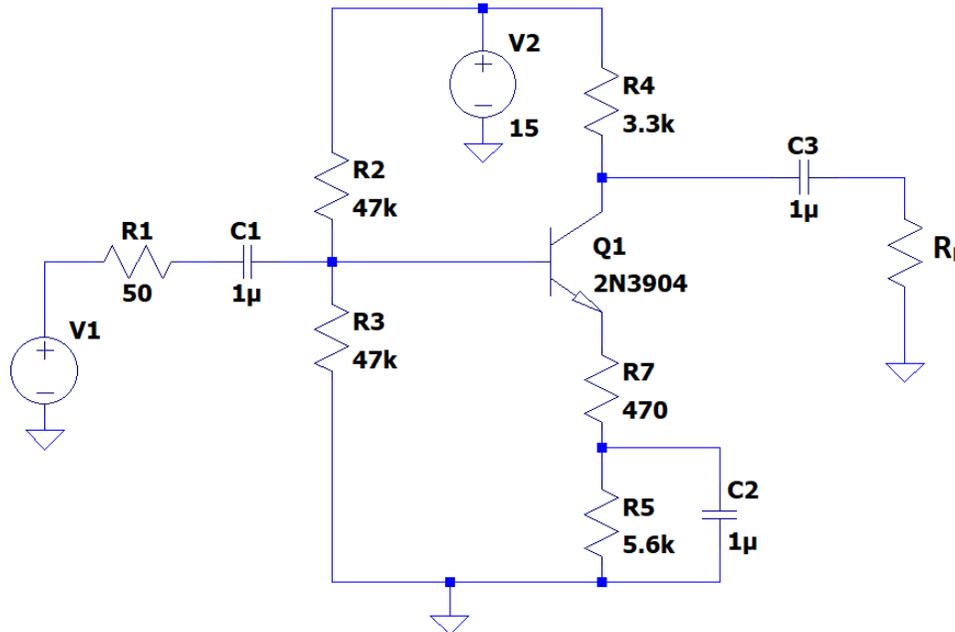

- 1) Perform a DC Analysis by hand (You may use the estimation technique as opposed to the Thevenin technique), Include a Load Line Analysis and show the Q-Point. Show all your work and include this in the writeup (you may include it hand written and stapled to this lab writeup).

Operational Parameters:

Operating Mode: _____ $I_c =$ _____ $V_{CE} =$ _____

Draw the Load Line and Qpoint:

CECS 311 - LAB 5
BJT Common Emitter Amplifier

- 2) Perform an AC Analysis by hand to arrive at your Amplifier Parameters, A_v , Z_{in} , Z_{out} . Show all your work and include this in the writeup (you may include it hand written and stapled to this lab writeup).

$A_v =$ _____ $Z_{in} =$ _____ $Z_{out} =$ _____

- 3) For $R_L = 10K$:

Draw the Circuit using the generic amplifier you derived the parameters for and attach a 10K Load Resistor. Make sure to include all input and output impedances.

Use this model to find V_{out} and V_{in} .

$V_{out} =$ _____ $V_{in} =$ _____

Calculated A_v (V_{out}/V_{in}) = _____

Error ($A_v - \text{Calculated } A_v$) = _____

Is the Calculated A_v similar to A_v from step 2? If not why, explain in one paragraph....

CECS 311 - LAB 5
BJT Common Emitter Amplifier

4) For $R_L = 1K$:

Draw the Circuit using the simplified generic amplifier you derived the parameters for and attach a 1K ohm Load Resistor. Make sure to include all input and output impedances.

Use this model to estimate V_{out} and V_{in} .

$V_{out} =$ _____ $V_{in} =$ _____

Calculated A_v (V_{out}/V_{in}) = _____

Error ($A_v - \text{Calculated } A_v$) = _____

Is the Calculated A_v similar to A_v from step 2? If not why, explain in one paragraph....

Part 2 – Simulation

1) Recreate this circuit under LT Spice and Simulate.

V_1 should equal a 500mVpk 1Khz ac voltage centered at 0v.

R_L is a load resistor, initially set this to 10k, we will change it later.

We are running 2 simulation cases, one with the amplifier driving a 10kohm load and another with 100ohm load. Please include a screenshot of the simulation for each case showing the **Waveform** and **Schematic**

1. Include 2 screenshots, one of the 10K load and the other of the 1K ohm load
2. Each waveform should show 5 cycles
3. Label the Input Signal: V_s
4. Label the Input Signal after attenuation by the Z_{out} of the source and Z_{in} of the Amplifier: V_{in}

CECS 311 - LAB 5
BJT Common Emitter Amplifier

5. Label the Output Signal after attenuation by Z_{out} of the Amplifier and Z_{in} of the Load:
 V_{out}
6. The Waveform should show V_s , V_{in} , V_{out}
7. Take measurements of the waveform using the LTspice measure tool and write these below.

Note: if you take the voltage probe after the output cap, they will all be referenced to 0v and will be easy to compare

	Case: $R_L = 10K$	Case: $R_L = 1K$	Calculated A_v
V_s (pk-pk)			
V_{in} (pk-pk)			
V_{out} (pk-pk)			

Part 3 – Breadboard Prototype

- Create a breadboard prototype of the CE Amplifier from Part 1, Use $R_L = 10K$
- Use the Function Generator to output 500mVpk at 1Khz, verify this directly using the oscilloscope before applying the signal to your amplifier!
- Place Ch1 of the Oscilloscope on V_{in} before the Amplifier
- Place Ch2 of the Oscilloscope on V_{out} before the Load
- Include a picture of the waveform from the oscilloscope and annotate with the pk-pk values measured on the oscilloscope, also note the 180deg Phase Shift
- Include a picture of the finished prototype running

Breadboard Measurements.

$V_{out} =$ _____ $V_{in} =$ _____

Calculated Gain: $A_v =$ _____