

CECS 211 – HW 1 - Solutions

For each problem, please show your entire work and submit via canvas. These problems are taken from chapters two and three from *J. Nilsson and S. Riedel, Electric Circuits, 10th*.

1.

P 2.11 [a] Using the passive sign convention and Ohm's law,

$$v = Ri = (3000)(0.015) = 45 \text{ V}$$


$$\text{[b]} P_R = \frac{v^2}{R} = \frac{45^2}{3000} = 0.675 = 675 \text{ mW}$$

[c] Using the passive sign convention with the current direction reversed,

$$v = -Ri = -(3000)(0.015) = -45 \text{ V}$$


$$P_R = \frac{v^2}{R} = \frac{-45^2}{3000} = 0.675 = 675 \text{ mW}$$

2.

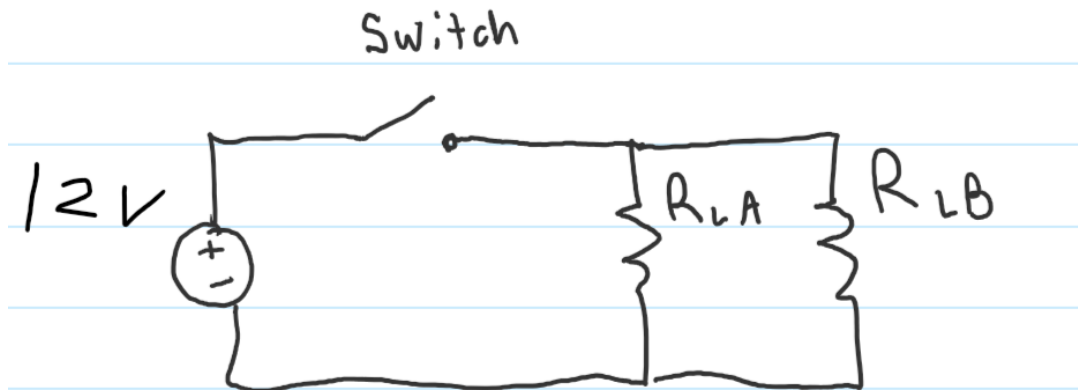

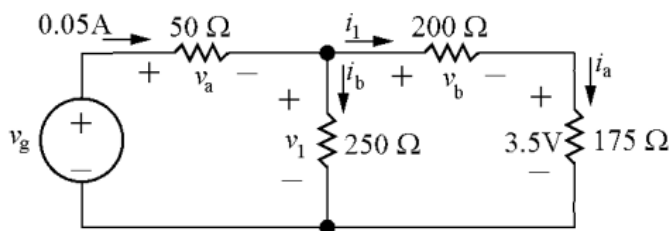3.

P 2.20 Label the unknown resistor voltages and currents:



[a] $i_a = \frac{3.5}{175} = 0.02 \text{ A}$ (Ohm's law)

$i_1 = i_a = 0.02 \text{ A}$ (KCL)

[b] $v_b = 200i_1 = 200(0.02) = 4 \text{ V}$ (Ohm's law)

$-v_1 + v_b + 3.5 = 0$ so $v_1 = 3.5 + v_b = 3.5 + 4 = 7.5 \text{ V}$ (KVL)


[c] $v_a = 0.05(50) = 2.5 \text{ V}$ (Ohm's law)

$-v_g + v_a + v_1 = 0$ so $v_g = v_a + v_1 = 2.5 + 7.5 = 10 \text{ V}$ (KVL)


[d] $p_g = v_g(0.05) = 10(0.05) = 0.5 \text{ W}$

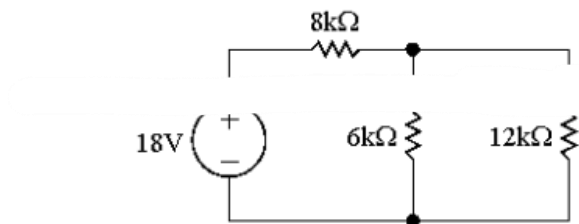4.


P 3.3 [a] The $5 \text{ k}\Omega$ and $7 \text{ k}\Omega$ resistors are in series. The simplified circuit is shown below:



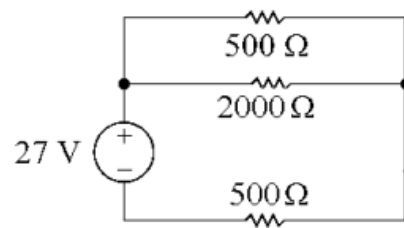
[b] The 800Ω and 1200Ω resistors are in series, as are the 300Ω and 200Ω resistors. The simplified circuit is shown below:



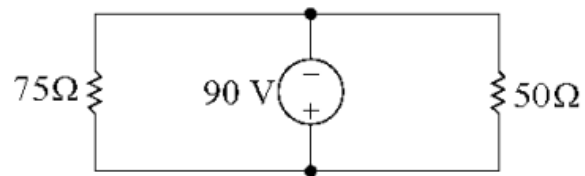
- [c] The $35\ \Omega$, $15\ \Omega$, and $25\ \Omega$ resistors are in series, as are the $10\ \Omega$ and $40\ \Omega$ resistors. The simplified circuit is shown below:



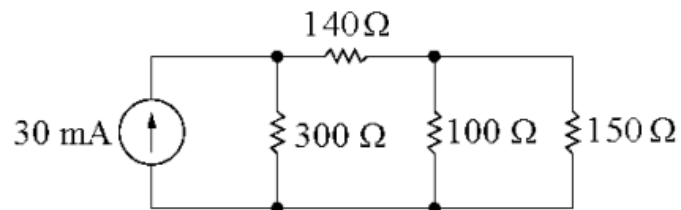
- [d] The $50\ \Omega$ and $90\ \Omega$ resistors are in series, as are the $80\ \Omega$ and $70\ \Omega$ resistors. The simplified circuit is shown below:



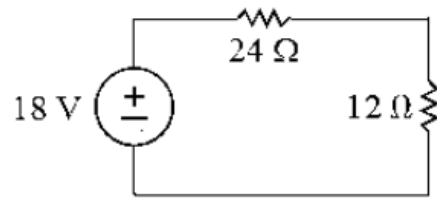
- P 3.4 [a] The $36\ \Omega$ and $18\ \Omega$ resistors are in parallel. The simplified circuit is shown below:



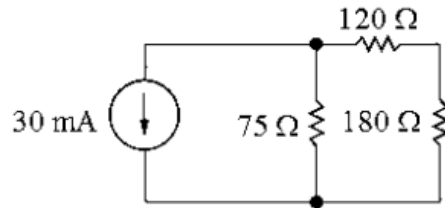
- [b] The $200\ \Omega$ and $120\ \Omega$ resistors are in parallel, as are the $210\ \Omega$ and $280\ \Omega$ resistors. The simplified circuit is shown below:



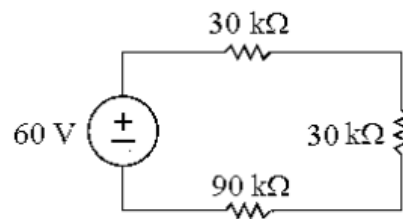- [c] The $100\ \text{k}\Omega$, $150\ \text{k}\Omega$, and $60\ \text{k}\Omega$ resistors are in parallel, as are the $75\ \text{k}\Omega$ and $50\ \text{k}\Omega$ resistors. The simplified circuit is shown below:



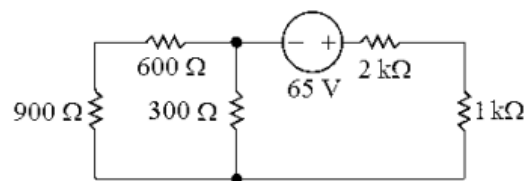- [d] The $750\ \Omega$ and $500\ \Omega$ resistors are in parallel, as are the $1.5\ \text{k}\Omega$ and $3\ \text{k}\Omega$ resistors. The simplified circuit is shown below:



- P 3.5 Always work from the side of the circuit furthest from the source. Remember that the current in all series-connected circuits is the same, and that the voltage drop across all parallel-connected resistors is the same.

[a] Circuit in Fig. P3.3(a):

$$\begin{aligned}R_{\text{eq}} &= [(7000 + 5000) \parallel 6000] + 8000 = 12,000 \parallel 6000 + 8000 \\&= 4000 + 8000 = 12 \text{ k}\Omega\end{aligned}$$

Circuit in Fig. P3.3(b):

$$\begin{aligned}R_{\text{eq}} &= [500 \parallel (800 + 1200)] + 300 + 200 = (500 \parallel 2000) + 300 + 200 \\&= 400 + 300 + 200 = 900 \Omega\end{aligned}$$

Circuit in Fig. P3.3(c):

$$R_{\text{eq}} = (35 + 15 + 25) \parallel (10 + 40) = 75 \parallel 50 = 30 \Omega$$

Circuit in Fig. P3.3(d):

$$\begin{aligned}R_{\text{eq}} &= ((70 + 80) \parallel 100) + 50 + 90 \parallel 300 = [(150 \parallel 100) + 50 + 90] \parallel 300 \\&= (60 + 50 + 90) \parallel 300 = 200 \parallel 300 = 120 \Omega\end{aligned}$$

- [b] Note that in every case, the power delivered by the source must equal the power absorbed by the equivalent resistance in the circuit. For the circuit in Fig. P3.3(a):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{18^2}{12,000} = 0.027 = 27 \text{ mW}$$

For the circuit in Fig. P3.3(b):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{27^2}{900} = 0.81 = 810 \text{ mW}$$

For the circuit in Fig. P3.3(c):

$$P = \frac{V_s^2}{R_{\text{eq}}} = \frac{90^2}{30} = 270 \text{ W}$$

For the circuit in Fig. P3.3(d):

$$P = I_s^2(R_{\text{eq}}) = (0.03)^2(120) = 0.108 = 108 \text{ mW}$$